



1

# Computer Organization

**Lab10** CPU(2) Minisys, Controller, ALU

2021 Spring term


wangw6@sustech.edu.cn

# Topics

- **CPU(2)**
  - **Controller**
  - **ALU**
- **Minisys**
  - **A Subset of MIPS32**
  - **The Assembler of Minisys**
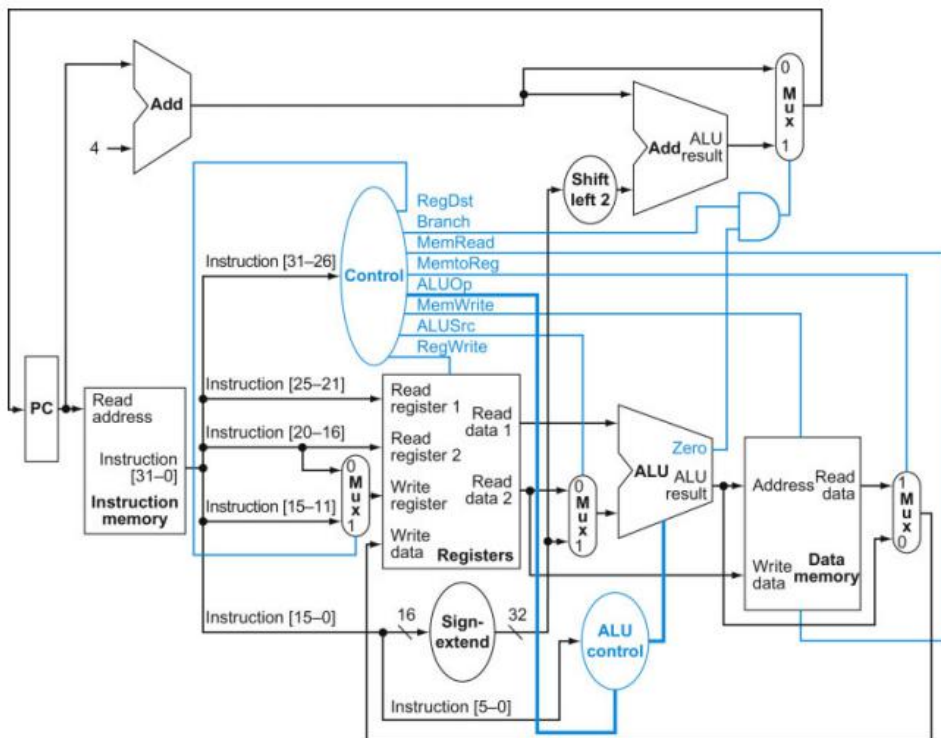
# Controller

Use opcode and funct code as input, generate the control signals which will be used in other modules.



Source: H&P textbook

## BASIC INSTRUCTION FORMATS

R	opcode	rs	rt	rd	shamt	funct
	31	26 25	21 20	16 15	11 10	6 5 0
I	opcode	rs	rt	immediate		
	31	26 25	21 20	16 15	0	
J	opcode	address				
	31	26 25				0


- part 1: get data from the instruction
  - address of registers: rs(Instruction[25:21]), rt(Instruction[20:16]) and rd(Instruction[15:11])
  - immediate(instruction[15:0])
  - shift mount(instruction[10:6])
  - address(instruction[25:0])
- part 2: get and analyze code in the instruction
  - opcode(instruction[31:26]), funct(bit[5:0])
  - generate control signals** to control the instruction execution

# Controller continued

Why a controller is needed?

Module	How To Process	Instructions and Comments
<b>Decoder</b>	Determine whether to write register or not	(lw), (R type instruction), (jal)
	Get the source of data to be written	1. data memory(lw) 2. alu(R) 3. address of instruction ->\$31 (jal)
	Get the address of register to be written	1. rt(lw) 2. rd(R) 3. 31 (jal)
<b>Memory</b>	Determine whether to write memory or not	(sw)
	Get the source of data to be written	register (sw)
<b>ALU</b>	Determine how to calculate the datas	add, sub, or, sll, sra, slt, branch ...
	Get the source of one operand from register or immediate extended	R(register), I(sign extended immediate)
<b>iFetch</b>	Determine how to update the value of PC register	1. (pc+4)+immediate(sign extended) (branch,I type)
		2. the value of \$31 register (jr, J type) 3. {(pc+4)[31:28],lableX[25:2],2'b00}
...	...	...

# Controller continued

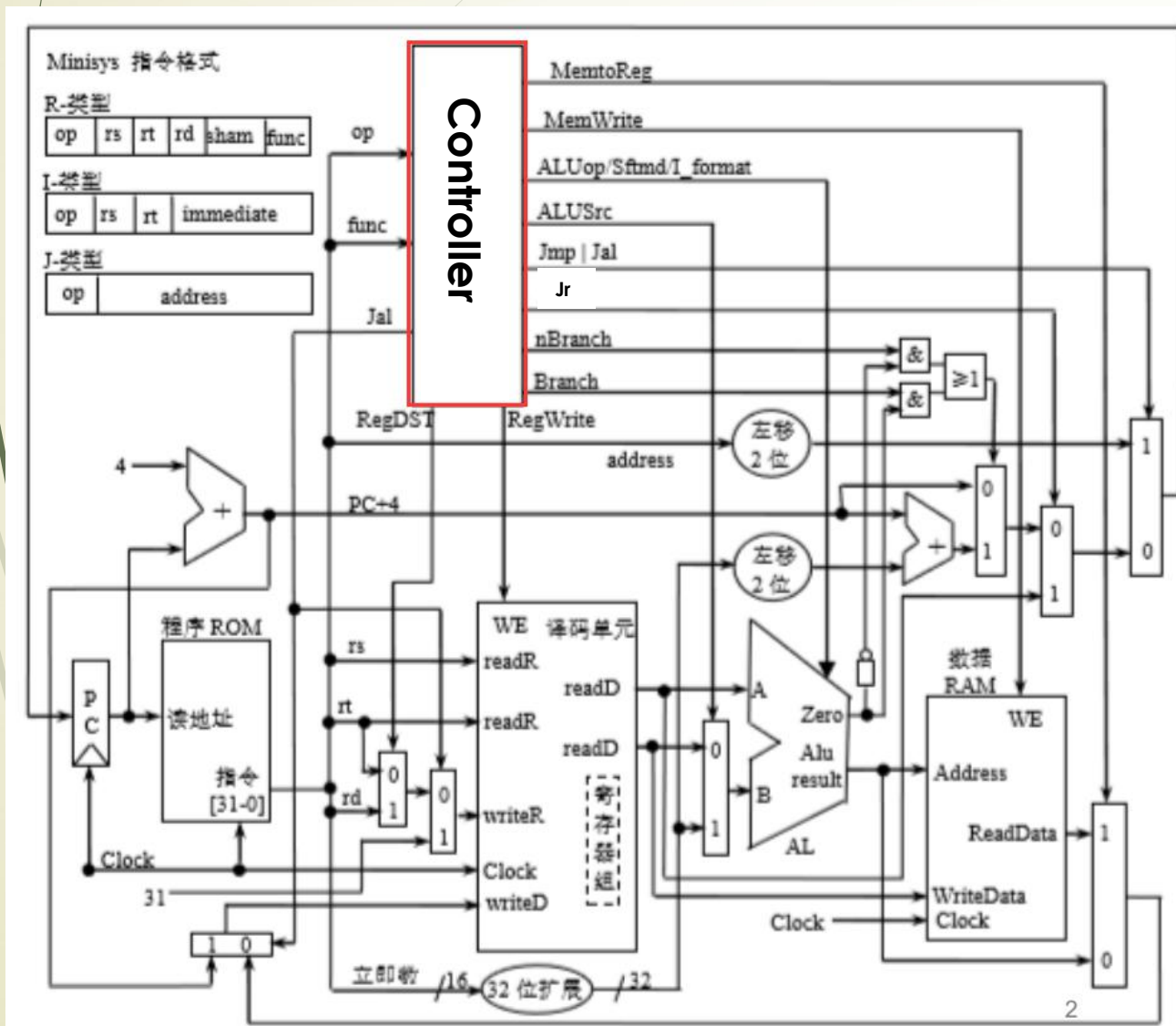

**Q1:** How to determine the type of the instruction, R, I or J?

**Q2:** What's the usage of function code in the instruction?

**Q3:** How to generate these control signals?

**Q4:** What's the type of the circuit about Controller? A combinational logic or a sequential logic?

# Minisys - A subset of MIPS32

Type	Name	funC (ins[5:0])
R	sll	00_0000
	sllv	00_0100
	srl	00_0010
	srlv	00_0110
	sra	00_0011
	srav	00_0111
	add	10_0000
	addu	10_0001
	sub	10_0010
	subu	10_0011
	and	10_0100
	or	10_0101
	xor	10_0110
	nor	10_0111
	slt	10_1010
	sltu	10_1011

Type	Name	opC (Ins[31:26])
I	beq	00_0100
	bne	00_0101
	lw	10_0011
	sw	10_1011
	addi	00_1000
	addiu	00_1001
	andi	00_1100
	ori	00_1101
	xori	00_1110
	slti	00_1010
	sltiu	00_1011
	lui	00_1111

Type	Name	opC (Ins[31:26])	funC
J	jr	00_0000	00_1000
	jump	00_0010	
	jal	00_0011	

NOTE:

The opC of R-Type instruction is 6'b00\_0000

Minisys is a subset of MIPS32.



MIPS\_Green\_Sheet.pdf

## BASIC INSTRUCTION FORMATS

<b>R</b>	opcode		rs		rt		rd		shamt		funct	
	31	26 25	21 20	16 15	11 10	6 5	0					
<b>I</b>	opcode		rs		rt		immediate					
	31	26 25	21 20	16 15	0							
<b>J</b>	opcode		address									
	31	26 25	0									

# Controller continued

## BASIC INSTRUCTION FORMATS

<b>R</b>	opcode	rs	rt	rd	shamt	funct
	31	26 25	21 20	16 15	11 10	6 5 0
<b>I</b>	opcode	rs	rt	immediate		
	31	26 25	21 20	16 15	0	
<b>J</b>	opcode	address				
	31	26 25	0			

## Controller

```

input[5:0] opcode;    // instruction[31..26]
input[5:0] Function_opcode;    // instructions[5..0]

output Jr;            // 1 indicates the instruction is "jr", otherwise it's not "jr"
output Jmp;           // 1 indicate the instruction is "j", otherwise it's not
output Jal;           // 1 indicate the instruction is "jal", otherwise it's not
output Branch;        // 1 indicate the instruction is "beq", otherwise it's not
output nBranch;       // 1 indicate the instruction is "bne", otherwise it's not
output RegDST;        // 1 indicate destination register is "rd", otherwise it's "rt"
output MemtoReg;       // 1 indicate read data from memory and write it into register
output RegWrite;      // 1 indicate write register, otherwise it's not
output MemWrite;       // 1 indicate write data memory, otherwise it's not
output ALUSrc;         // 1 indicate the 2nd data is immediate (except "beq", "bne")
output I_format;       // 1 indicate the instruction is I-type but isn't "beq", "bne", "LW" or "SW"
output Sftmd;          // 1 indicate the instruction is shift instruction

// if the instruction is R-type or I_format, ALUOp is 2'b10; if the instruction is "beq" or "bne", ALUOp is 2'b01;
// if the instruction is "lw" or "sw", ALUOp is 2'b00;

output[1:0] ALUOp;

```



# Controller continued

“Jr” is used to identify whether the instruction is jr or not.

$$\text{Jr} = ((\text{Function\_opcode} == 6'b001000) \&\& (\text{Opcode} == 6'b000000)) ? 1'b1 : 1'b0;$$

opCode	001101	001001	100011	101011	000100	000010	000000
Instruction	ori	addiu	lw	sw	beq	j	R-format
RegDST	0	0	0	x	x	x	1

“RegDST” is used to determine the destination in the register file which is determined by rd(1) or rt(0)

$$\text{R\_format} = (\text{Opcode} == 6'b000000) ? 1'b1 : 1'b0;$$

$$\text{RegDST} = \text{R\_format};$$

opCode	001xxx	000000	100011	101011	000011	000010	000000
Instruction	I-format	jr	lw	sw	jal	j	R-format
RegWrite	1	0	1	x	1	x	1

“RegWrite” is used to determine whether to write registe(1) or not(0).

$$\text{RegWrite} = (\text{R\_format} || \text{Lw} || \text{Jal} || \text{I\_format}) \&\& !(\text{Jr})$$



# Controller continued

Type	Name	opC (Ins[31:26])
I	beq	00_0100
	bne	00_0101
	lw	10_0011
	sw	10_1011
	addi	00_1000
	addiu	00_1001
	andi	00_1100
	ori	00_1101
	xori	00_1110
	slti	00_1010
	sltiu	00_1011
	lui	00_1111

**"I\_format"** is used to identify if the instruction is I\_type (except for beq, bne, lw and sw).  
e.g. addi, subi, ori, andi...

**I\_format** = (Opcode[5:3]==3'b001)?1'b1:1'b0;

Instruction	ALUOp
lw	00
sw	00
beq,bne	01
R-format	10
I-format	10

**"ALUOp"** is used to code the type of instructions described in the table on the left hand.

**ALUOp** = {(R\_format || I\_format),(Branch || nBranch)};

Type	Name	funC (ins[5:0])
R	sll	00_0000
	sllv	00_0100
	srl	00_0010
	srlv	00_0110
	sra	00_0011
	srav	00_0111

**"Sftmd"** is used to identify whether the instruction is shift cmd or not.  
**Sftmd** = (((Function\_opcode==6'b000000)||((Function\_opcode==6'b000010)

||((Function\_opcode==6'b000011)||((Function\_opcode==6'b000100)

||((Function\_opcode==6'b000110)||((Function\_opcode==6'b000111))  
&& R\_format)? 1'b1:1'b0;

# Practice1

- 1. Complete the Controller
- 2. Verify its function by simulation according to the following table.

TIPS: Minisys1 Assemblerv2.2 could help to generate the corresponding instructions

time(ns)	opcode	function_opcode	instruction
0	6'h00	6'h20	add rd,rs,rt //RegDST=1, RegWrite=1, ALUSrc=0, ALUOp=10
200	6'h00	6'h08	jr rs //RegDST=1, RegWrite=0, ALUSrc=0, ALUOp=10, jr=1,
400	6'h08	6'h08	addi rt,rs,imm //RegDST=0, RegWrite=1, ALUSrc=1, I_format=1
600	6'h23	6'h08	lw rt,imm(rs) //RegDST=0, RegWrite=1, ALUSrc=1, ALUOp=00, MemtoReg=1
800	6'h2b	6'h08	sw rt,imm(rs) //RegDST=0, RegWrite=0, ALUSrc=1, ALUOp=00, MemtoReg=0, MemWrite=1
1050	6'h04	6'h08	beq rs,rt,label //RegDST=0, RegWrite=0, ALUSrc=0, ALUOp=01, Branch=1
1250	6'h05	6'h08	bne rs,rt,label //RegDST=0, RegWrite=0, ALUSrc=0, ALUOp=01, Branch=0, nBranch=1
1500	6'h02	6'h08	j label //RegDST=0, RegWrite=0, ALUSrc=0, ALUOp=00, Branch=0, nBranch=0, Jmp=1
1700	6'h03	6'h08	jal label //RegDST=0, RegWrite=1, ALUSrc=0, ALUOp=00, Branch=0, nBranch=0, Jmp=0, Jal=1
1950	6'h00	6'h02	srl rd,rt,shamt //RegDST=1, RegWrite=1, ALUSrc=0, ALUOp=10, sftmd=1

Minisys1Assemblerv2.2(An Asambler on Minisys) could be found at below address:

<https://sakai.sustech.edu.cn/portal/site/d50211ea-1586-4344-9d92-a6c42eb7f4e0/tool/b47e4c13-4220-4f61-b881-a211abee2a96?panel=Main>

# Tips: a reference to build a testbench

```

module control32_tb
    //reg type variables are use for binding with input ports
    reg [5:0] Opcode,Function_opcode;
    //wire type variables are use for binding with output ports
    wire [1:0] ALUOp;
    wire Jr,RegDST,ALUSrc,MemtoReg,RegWrite,MemWrite,Branch,nBranch,Jmp,Jal,I_format,Sftmd;

    //instance the module "control32", bind the ports
    control32 c32
    (Opcode,Function_opcode,
    Jr,Branch,nBranch,Jmp,Jal,
    RegDST,MemtoReg,RegWrite,MemWrite,
    ALUSrc,ALUOp,Sftmd,I_format);

    initial begin
        //an example: #0 add $3,$1,$2. get the machine code of 'add $3,$1,$2'
        // step1: edit the assembly code, add "add $3,$1,$2"
        // step2: open the assembly code in Minisys1A assembler, do the assembly procession
        // step3: open the "output/prgmips32.coe" file, find the related machine code of 'add $3,$1,$2'
        //in "0x00221820", 'Opcode' is 6'h00,'Function_opcode' is 6'h20
        Opcode = 6'h00;
        Function_opcode = 6'h20;

        #200 //...

    end
endmodule

```

Tips:  
The codes on Page 6 is another chooice

# How To Use “Minisys1 Assembler v2.2 ”


- Step1. **Open** the assembly **source** file



- Step2. “工程”-» “**64KB**” (the size of Instruction memory and data memory)  
-» “**A 汇编**”



 - Step3. The coe files could be found at the sub-directory: “**output**”
  - The initial data of data memory could be found in file “dmem32.coe”
  - The machine code of Minisys instruction could be found in the file “**prgmip32.coe**”



Following screenshot is an example, the machine code is recorded in **hexadecimal**.


```

1 memory_initialization_radix = 16;
2 memory_initialization_vector =
3 34010001,
4 34020002,
5 34030003,
6 34040004,
7 34050005,
8 34060006,
9 34070007,
10 34080008,
11 34090009,
12 340a000a,

```
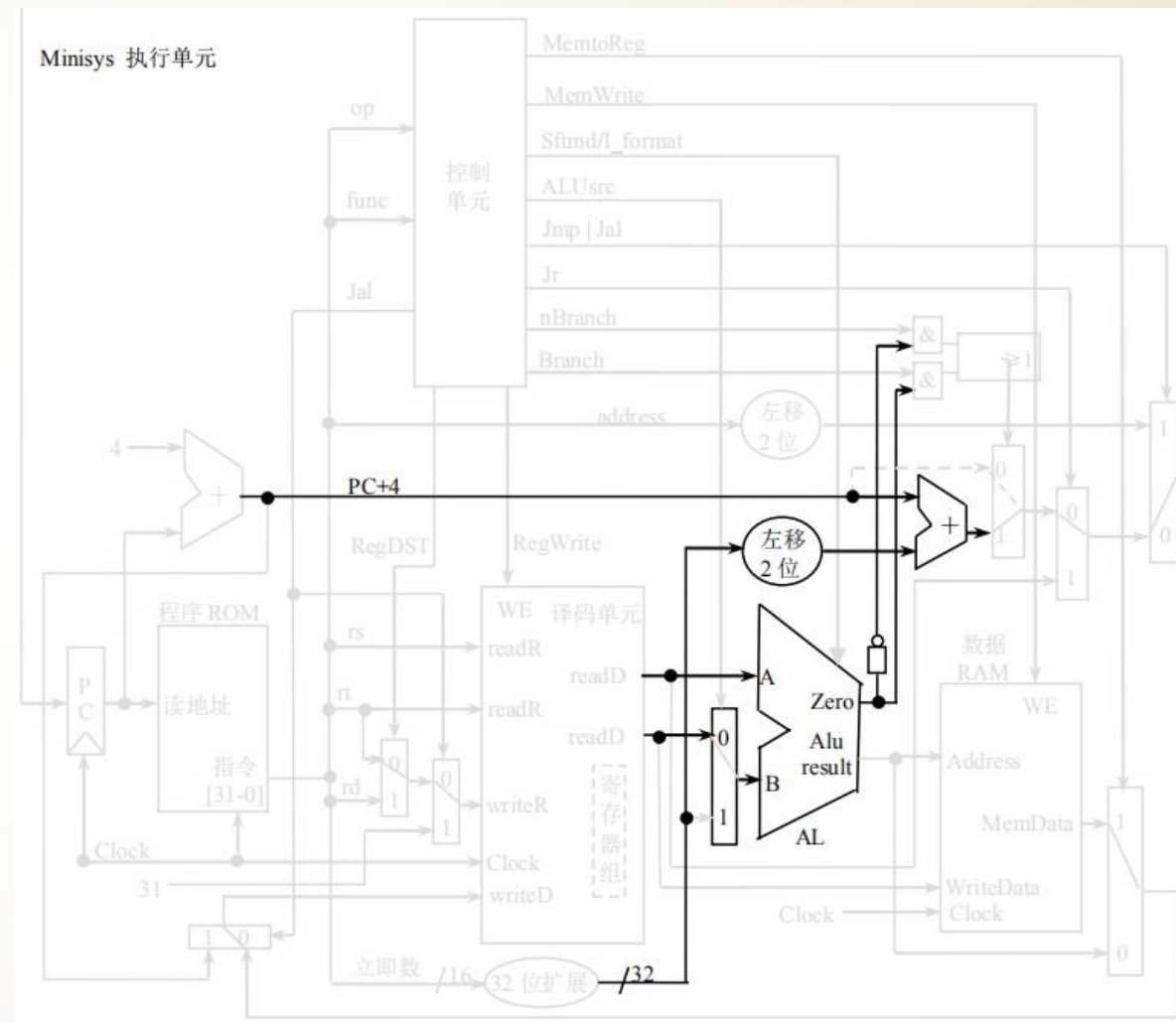
# ALU

- ▶ Determine the function and the inputs and outputs
- ▶ A MUX for operand selection
- ▶ **Operation**
  - ▶ ALU\_control
  - ▶ Operation
    - ▶ **Arithmetic and Logic** calculation
    - ▶ **Shift** calculation
    - ▶ **Special** calculation (slt, lui)
    - ▶ **Address** calculation



```
module Executs32 ( );  
// from decoder  
input[31:0] Read_data_1; //the source of Ainput  
input[31:0] Read_data_2; //one of the sources of Binput  
input[31:0] Sign_extend; //one of the sources of Binput  
  
// from ifetch  
input[5:0] Function_opcode; //instructions[5:0]  
input[5:0] Opcode; //instruction[31:26]  
input[4:0] Shamt; // instruction[10:6], the amount of shift bits  
input[31:0] PC_plus_4; // pc+4  
  
// from controller  
input[1:0] ALUOp; //{ (R_format | I_format) , (Branch | nBranch) }  
input ALUSrc; // 1 means the 2nd operand is an immediate (except beq, bne)  
input I_format; // 1 means I-Type instruction except beq, bne, LW, SW  
input Sftmd; // 1 means this is a shift instruction  
input Jr; // 1 means this is a jr instruction
```



# Outputs And Variable of ALU continued

```
output Zero;                // 1 means the ALU_reslut is zero, 0 otherwise
output[31:0]    reg ALU_Result;    // the ALU calculation result
output[31:0]    Addr_Result;    // the calculated instruction address
```

```
wire[31:0]    Ainput,Binput;        // two operands for calculation

wire[5:0]    Exe_code;    // use to generate ALU_ctrl. (I_format==0) ? Function_opcode : { 3'b000 , Opcode[2:0] };
wire[2:0]    ALU_ctl;    // the control signals which affact operation in ALU directly
wire[2:0]    Sftm;        // identify the types of shift instruction, equals to Function_opcode[2:0]


reg[31:0]    ALU_output_mux;        // the result of arithmetic or logic calculation
reg[31:0]    Shift_Result;        // the result of shift operation

wire[32:0]    Branch_Addr;        // the calculated address of the instruction, Addr_Result is Branch_Addr[31:0]
```


 
# The Selection On Operand2


- Two operands: Ainput and Binput.
- Binput** is the output of 2-1 MUX:
  - "**Sign\_extend**" and "**Read\_data\_2**" are from decoder.
  - The output of the MUX is determined by "**ALUSrc**".



```
input[31:0] Read_data_1; // from decoder
input[31:0] Read_data_2; // from decoder
input[31:0] Sign_extend; // from decoder
input      ALUSrc;       // from controller, 1 means the operand2 is an immediate

assign Ainput = Read_data_1;
assign Binput = (ALUSrc == 0) ? Read_data_2 : Sign_extend[31:0];
```

# ALU\_ctrl

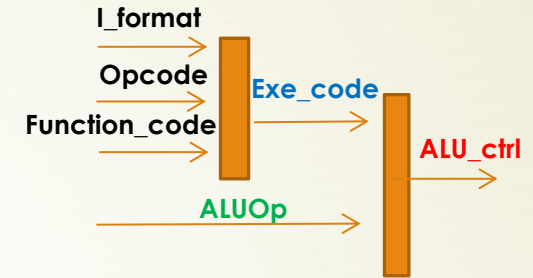

## Design :


- lots of operations need to be processed in ALU
- to reduce the burden of the controller, the controller and ALU produce control signals which affect the alu operation together

## Implements :

- ALUOp** (1st level control signal) : **generated by Controller** ( the basic relationship between instruction and operation)
  - bit1 to identify if the instruction is R\_format/ I\_format, otherwise means neither
  - bit0 to identify if the instruction is beq/ bne, otherwise means neither
  - ALUOp = { (R\_format || I\_format) , (Branch || nBranch) }**
- Exe\_code** (2nd level control signal) : **generated by ALU**
  - according to the instruction type( I-format or not)
  - Exe\_code = (I\_format==0) ? Function\_opcode : { 3'b000 , Opcode[2:0] };**  
 tips: **Opcode** is **instruction[31:26]**, **function\_opcode** is **instruction[5:0]**  
 tips: **I\_format** is 1 means this is the **I-type instruction** except **beq, bne, lw** and **sw**.
- ALU\_ctrl** : **generated by ALU** based on **ALUOp** and **Exe\_code**  
**specify most of the operation details in ALU**

# ALU\_ctrl continued

Exe_code[3..0]	ALUOp[1..0]	ALU_ctl[2..0]	指令助记符
0100	10	000	and, andi
0101	10	001	or, ori
0000	10	010	add, addi
xxxx	00	010	lw, sw
0001	10	011	addu, addiu
0110	10	100	xor, xori
0111	10	101	nor, lui
0010	10	110	sub, slti
xxxx	01	110	beq, bne
0011	10	111	subu, sltiu
1010	10	111	slt
1011	10	111	sltu

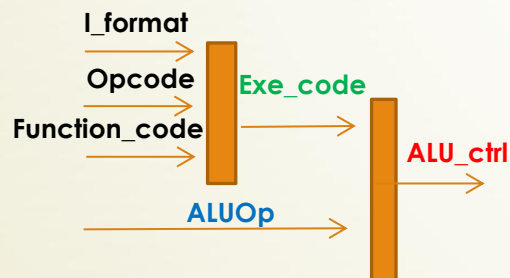

**ALUOp** =  
 { (R\_format || I\_format) , (Branch || nBranch) }

**Exe\_code** =  
 (I\_format==0) ?  
 Function\_opcode : { 3'b000 , Opcode[2:0] };  
 // Function\_opcode equals to Instruction[5:0]  
 // Opcode equals to Instruction[31:26]

```
assign ALU_ctl[0] = (Exe_code[0] | Exe_code[3]) & ALUOp[1];
```

```
assign ALU_ctl[1] = ((!Exe_code[2]) | (!ALUOp[1]));
```

```
assign ALU_ctl[2] = (Exe_code[1] & ALUOp[1]) | ALUOp[0];
```

# ALU\_ctrl continued

## Type1

### The same operation in ALU with different operand source

sometimes the instructions share the same calculation operation but with different operand source, such as “and” and “andi”, “addu” and “addui”.

the same operation but  
different operand source:

**ALU\_ctrl** is same

**add** vs **addi**

**addu** vs **addiu**

**and** vs **andi**

**or** vs **ori**

**xor** vs **xori**

**slt** vs **sltu** vs **sltiu**

Exe_code[3..0]	ALUOp[1..0]	ALU_ctrl[2..0]	指令助记符
0100	10	000	and, andi
0101	10	001	or, ori
0000	10	010	add, addi
xxxx	00	010	lw, sw
0001	10	011	addu, addiu
0110	10	100	xor, xori
0111	10	101	nor, lui
0010	10	110	sub, slti
xxxx	01	110	beq, bne
0011	10	111	subu, sltiu
1010	10	111	slt
1011	10	111	sltu

# ALU\_ctrl continued

## ▶ Type2

The same operation in ALU with different destination

- ▶ The **ALU\_ctrl** code is same for both "lw", "sw" and "add":
  - ▶ the operation of "lw" and "sw" in ALU is calculation the address based on the base address and offset which is same as in "add" operation.

Exe_code[3..0]	ALUOp[1..0]	ALU_ctrl[2..0]	指令助记符
0100	10	000	and, andi
0101	10	001	or, ori
0000	10	010	add, addi
xxxx	00	010	lw, sw
0001	10	011	addu, addiu
0110	10	100	xor, xori
0111	10	101	nor, lui
0010	10	110	sub, slti
xxxx	01	110	beq, bne
0011	10	111	subu, sltiu
1010	10	111	slt
1011	10	111	sltu

# ALU\_ctrl continued

## ▶ Type2 continued

The same operation in ALU with different destination

- ▶ “beq”, “bne” vs “sub”:
  - ▶ the destination of “beq” and “bne” is addr\_reslut not the “ALU\_reslut”
- ▶ “subu” vs “slt”, “sltu”
  - ▶ the destination of “slt” and “sltiu” is Zero. **I\_format** is used here to distinguish these two types
- ▶ “sub” vs “slt”, “subu” vs “sltiu”:
  - ▶ same as upper instruction, **Function\_opcode**(3)=1 of slt and sltu **could be used as distinction**

Exe_code[3..0]	ALUOp[1..0]	ALU_ctl[2..0]	指令助记符
0100	10	000	and, andi
0101	10	001	or, ori
0000	10	010	add, addi
xxxx	00	010	lw, sw
0001	10	011	addu, addiu
0110	10	100	xor, xori
0111	10	101	nor, lui
0010	10	110	sub, slti
xxxx	01	110	beq, bne
0011	10	111	subu, sltiu
1010	10	111	slt
1011	10	111	sltu

## ALU\_ctrl continued

### ► Type3

**Some** instructions' **ALU\_ctrl code** is the same as others, but with **different operation** in ALU. For these instructions, make sure they can be identified to avoid wrong operations:

- **shift** instructions: could be identified by the input port "**sftmd**"
- **lui** : whose ALU\_ctrl code is the same as "nor", but could be identified by "**I\_format**"
- **jr** : could be identified by the input port "jr", not execute in ALU
- **j** : could be identified by the input port "jmp", not execute in ALU
- **jal** : could be identified by the input port "jal", execute in both ifetch and ALU



## Practice2-1 Arithmetic and Logic calculation

- Complete the following code according to the table on the right hand

```

reg[31:0] ALU_output_mux;
always @(ALU_ctl or Ainput or Binput)
begin
case (ALU_ctl)
    3'b000:ALU_output_mux =? ? ?
    3'b001:ALU_output_mux =? ? ?
    3'b010:ALU_output_mux =? ? ?
    3'b011:ALU_output_mux =? ? ?
    3'b100:ALU_output_mux =? ? ?
    3'b101:ALU_output_mux =? ? ?
    3'b110:ALU_output_mux =? ? ?
    3'b111:ALU_output_mux =? ? ?
    default:ALU_output_mux = 32'h00000000;
endcase
end

```

Exe_code[3..0]	ALUOp[1..0]	ALU_ctl[2..0]	指令助记符
0100	10	000	and,andi
0101	10	001	or,ori
0000	10	010	add,addi
xxxx	00	010	lw,sw
0001	10	011	addu,addiu
0110	10	100	xor,xori
0111	10	101	nor,lui
0010	10	110	sub,slti
xxxx	01	110	beq, bne
0011	10	111	subu,sltiu
1010	10	111	slt
1011	10	111	sltu

# Shift Operation

- There are 6 shift instructions, listed in the table on the left hand below
- Ainput, Binput/shamt are the operand of shift operation

sftm[2:0]	process
3'b000	sll rd, rt, shamt
3'b010	srl rd, rt, shamt
3'b100	sllv rd, rt, rs
3'b110	srlv rd, rt, rs
3'b011	sra rd, rt, shamt
3'b111	srav rd, rt, rs
other	not shift

```

input[4:0]  Shamt;    // from ifetch, instruction[10:6], its value is shift amount
input      Sftmd;    // from controller, 1 means this is a shift instruction
input[5:0]  Function_opcode; //r-type instruction, instruction[5:0]
reg[31:0]   Shift_Result; //the result of shift operation
wire[2:0]   Sftm;

```

```

assign Sftm = Function_opcode[2:0]; //the code of shift operations

```

# Practice2-2 Shift Operation

Complete the following code, taking the table on the left hand as reference

sftm[2:0]	process
3'b000	sll rd, rt, shamt
3'b010	srl rd, rt, shamt
3'b100	sllv rd, rt, rs
3'b110	srlv rd, rt, rs
3'b011	sra rd, rt, shamt
3'b111	srav rd, rt, rs
other	not shift

```

always @* begin // six types of shift instructions
    if(Sftmd)
        case(Sftm[2:0])
            3'b000:Shift_Result = Binput << Shamt;           //Sll rd,rt,shamt 00000
            3'b010:Shift_Result = ???;                       //Srl rd,rt,shamt 00010
            3'b100:Shift_Result = Binput << Ainput;           //Sllv rd,rt,rs 000100
            3'b110:Shift_Result = ???;                       //Srlv rd,rt,rs 000110
            3'b011:Shift_Result = ???;                       //Sra rd,rt,shamt 00011
            3'b111:Shift_Result = ???;                       //Srav rd,rt,rs 00111
            default:Shift_Result = Binput;
        endcase
    else
        Shift_Result = Binput;
    end
end

```

# Get the Output of ALU

The operations of ALU include:

- ▶ 1) do the setting type instruction ( slt、sltu、slti and sltiu )
  - ▶ get ALU\_output\_mux, and set the value of the output port "Zero"
- ▶ 2) do the lui operation
- ▶ 3) do the shift operation
  - ▶ get shift amount, do the shift operation according to the "Sftm", set the value of the output port "Shift\_Result"
- ▶ 4) do the basic arithmetic and logic calculation
  - ▶ get ALU\_output\_mux, set its value to the output port "ALU\_result"

**Tips:** Exe\_code[3..0]、ALUOp[1..0] and ALU\_ctl[2..0] are used to identify the types of operation

# Get the Output of ALU continued

```
always @* begin
    //set type operation (slt, slti, sltu, sltiu)
    if(((ALU_ctl==3'b111) && (Exe_code[3]==1))||((ALU_ctl[2:1]==2'b11) && (I_format==1))
        ALU_Result = (Ainput-Binput<0)?1:0;

    //lui operation
    else if((ALU_ctl==3'b101) && (I_format==1))
        ALU_Result[31:0]={Binput[15:0],{16{1'b0}}};

    //shift operation
    else if(Sftmd==1)
        ALU_Result = Shift_Result ;

    //other types of operation in ALU (arithmetic or logic calculation)
    else
        ALU_Result = ALU_output_mux[31:0];
end
```

## Practice2-3 Complete ALU

- ▶ The values of “**Addr\_result**” and “**zero**” are still not determined.  
Complete the ALU code.

- ▶ “**zero**” is a signal used by “**ifetch**” to determine whether to use the value of “**Addr\_reslut**” to update **PC** register or not.

TIPS: Minisys only support “beq” and “bne” in the conditional jump instruction.

- ▶ “**Addr\_result**” is calculated by ALU when the instruction is “**beq**” or “**bne**”.

TIPS: Addr\_reslut should be the sum of pc+4 and the immediate in the instruction.

## Practice2-4 Function Verification on ALU

Build a testbench to verify the function of ALU. (TIPS: p11 could be a reference)  
 Take the testcases described in bellow table as reference  
 More testcases are suggested for function verification

Time (ns)	Instruction	A input	B input	Results(includes 'Zero')
0	add	0x5	0x6	ALU_Result = 0x0000_000b, Zero=1'b0
200	addi	0xffff_ff40	0x3	ALU_Result = 0xffff_ff43, Zero=1'b0
400	and	0x0000_00ff	0x0000_0ff0	ALU_Result = 0x0000_00f0, Zero=1'b0
600	sll	0x0000_0002	0x3	ALU_Result = 0x0000_0010, Zero=1'b0
800	lui	0x0000_0040	0x10 (16)	ALU_Result = 0x0040_0000, Zero=1'b0
1000	beq	The value of Ainput is same with that of Binput. Zero = 1'b1 <b>Addr_Result:</b> the address of current instruction is 0x0000_0006, the offset is 0x0000_0004, 'Addr_Result' should be 0x0000_000a		