



1

# Computer Organization

**Lab9** CPU Design1: Decoder and DataMemory

2021 Spring term

wangw6@sustech.edu.cn

# Topics

- CPU Design(1)
  - ISA
- Data Path(1)
  - Decoder
  - Data Memory
    - Customize block memory IP core
    - Instance IP core to build Data Memory

# ISA-MIPS

## 1. Immediate addressing




## 2. Register addressing





Registers

Register


## 3. Base addressing

 



Memory

  


## 4. PC-relative addressing

 



Memory

  

## 5. Pseudodirect addressing

 

Memory

  

## BASIC INSTRUCTION FORMATS

R	opcode	rs	rt	rd	shamt	funct
	31	26 25	21 20	16 15	11 10	6 5 0
I	opcode	rs	rt	immediate		
	31	26 25	21 20	16 15	0	
J	opcode	address				
	31	26 25	0			

## MIPS addressing


- 1. immediate addressing:
  - addi \$s0,\$s1,5 **【I】**
- 2. register addressing:
  - add \$s0,\$s1,\$s2 **【R】**
- 3. base addressing:
  - lw \$s0,0 (\$s1) **【I】**
- 4. pc-relative addressing
  - bne \$s0,\$s1,EXIT **【I】**
- 5. psudo-directive addressing
  - j EXIT **【J】**

# How CPU works

- **Fetch** the instruction from the **instruction memory** according to the value of the **PC** register
- **Analyze** the instruction to get how to process the data
- **Execute** the instruction
  - R type :
    - [add] : **find** the **register** and **read** its value, do the **arithmetic calculation** , **write** the **register**
  - I type :
    - [addi]: same as add except one of operands is from the immediate number of the instruction
    - [branch]: **find** the register and **read** its value, do the **comparation** and **write** the **PC register** with the target address(pc relative addressing)
    - [load/store]: **find** source data from the **register/memory**, **read** its value to **wirte** the target place
  - J type :
    - [ j ] : **write** the **PC** register with the target address(presdo-directory addressing)
    - [ jr ] : **write** the **PC** register with the value of **\$31**
    - [ jal ] : **write** **\$31** and the **PC** register

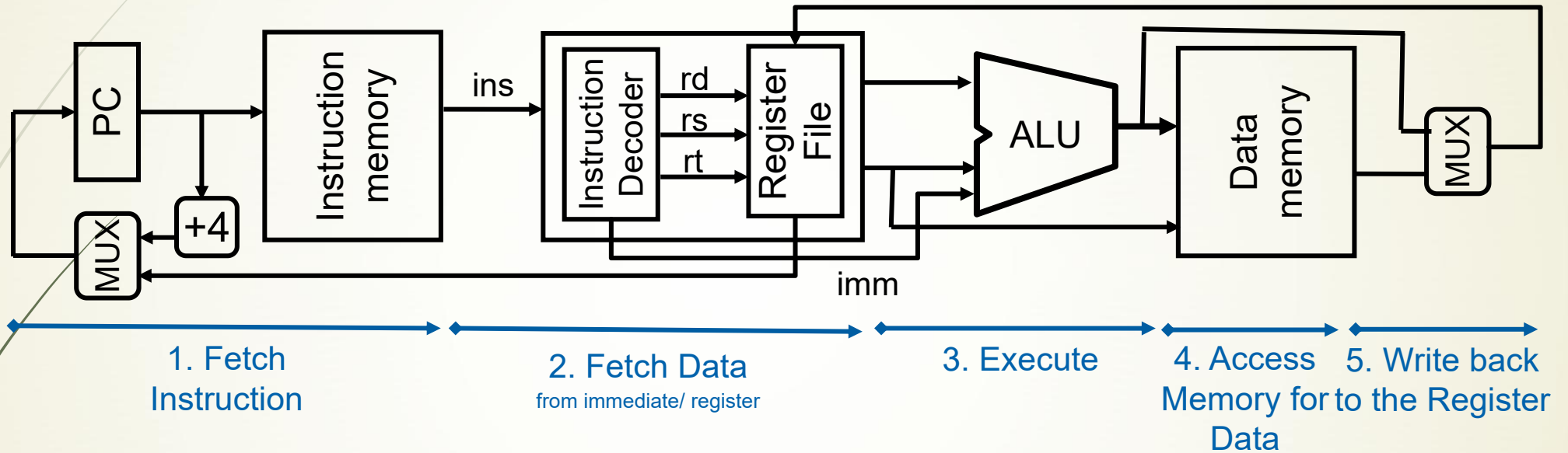
# Core Modules in CPU

reference from Minisys, a little modification



	Instruction fetch	Data Fetch	Instruction Execute	Memory Access	Register WriteBack
add[R]	Y	Y	Y		Y
store[I]	Y	Y	Y	Y	
load[I]	Y	Y	Y	Y	Y
branch[I]	Y	Y	Y		
jump[J]	Y	Y	Y		
jal [J]	Y	Y	Y		

# Decoder

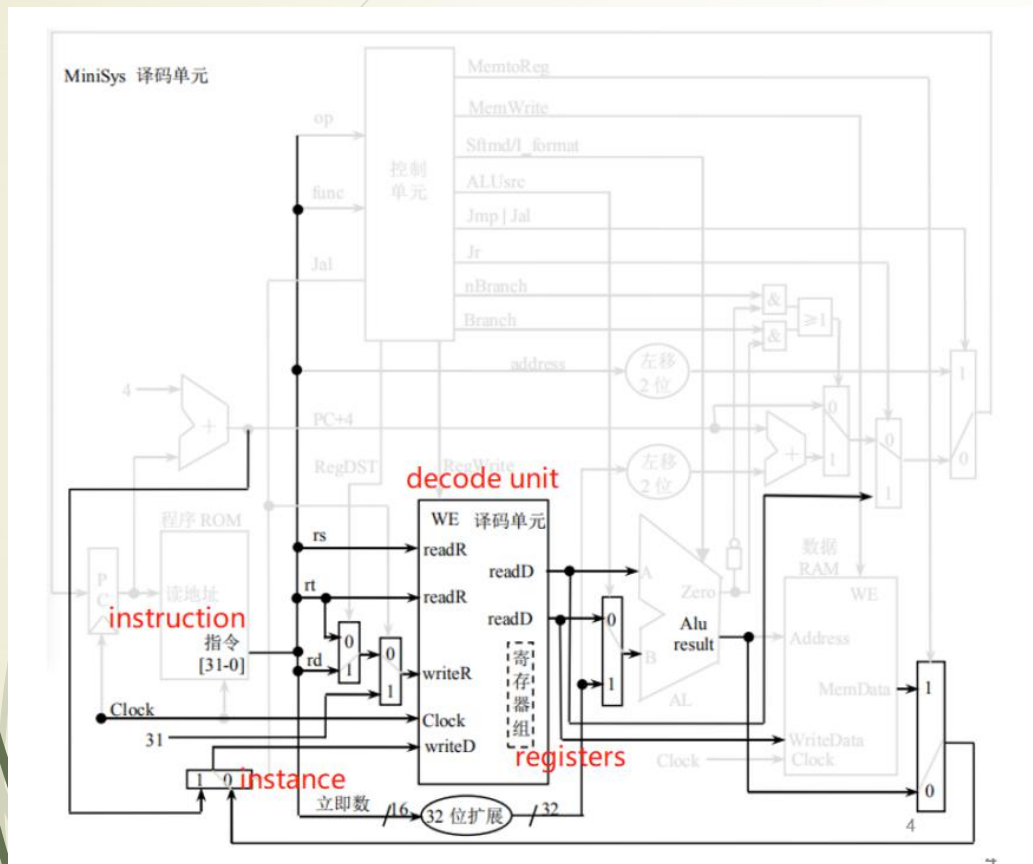

## Get data from the instruction directly or indirectly

opcode, function code : how to get data, where to get data

immediate data in the instruction ([15:0]), (e.g. immi = Instruction[15:0]) need to be **signextended to 32bits**

data in the register, the address of the register is coded in the instruction. e.g. rs = Instruction[25:21];

data in the memory, the address of the memory unit need to be calculated by ALU with base address stored in the register and offset as immediate data in the instruction

## Read/Write data from/to Register File

### BASIC INSTRUCTION FORMATS

R	opcode	rs	rt	rd	shamt	funct
	31	26 25	21 20	16 15	11 10	6 5 0
I	opcode	rs	rt	immediate		
	31	26 25	21 20	16 15	0	
J	opcode	address				
	31	26 25	0			

# Decoder continued

## Register File

## Inputs

### read address

- [R] add: rs,rt
- [J] jr : [31]

### write address

- [R] add: rd
- [J] jal : [31]
- [I] addi: rt

### write data

- [R] add: alu\_result
- [J] jal : pc+4
- [I] load: data from memory

### control signal

- [R] /[I]/[J] writeRegister
- [J]: jal
- [I] : memToReg
- [R]/[I]: rd vs rt


## BASIC INSTRUCTION FORMATS

<b>R</b>	opcode	rs	rt	rd	shamt	funct
	31 26 25	21 20	16 15	11 10	6 5	
<b>I</b>	opcode	rs	rt	immediate		
	31 26 25	21 20	16 15			
<b>J</b>	opcode	address				
	31 26 25					

## Register File

## Outputs


- read data1
- read data2
- extendedImmi

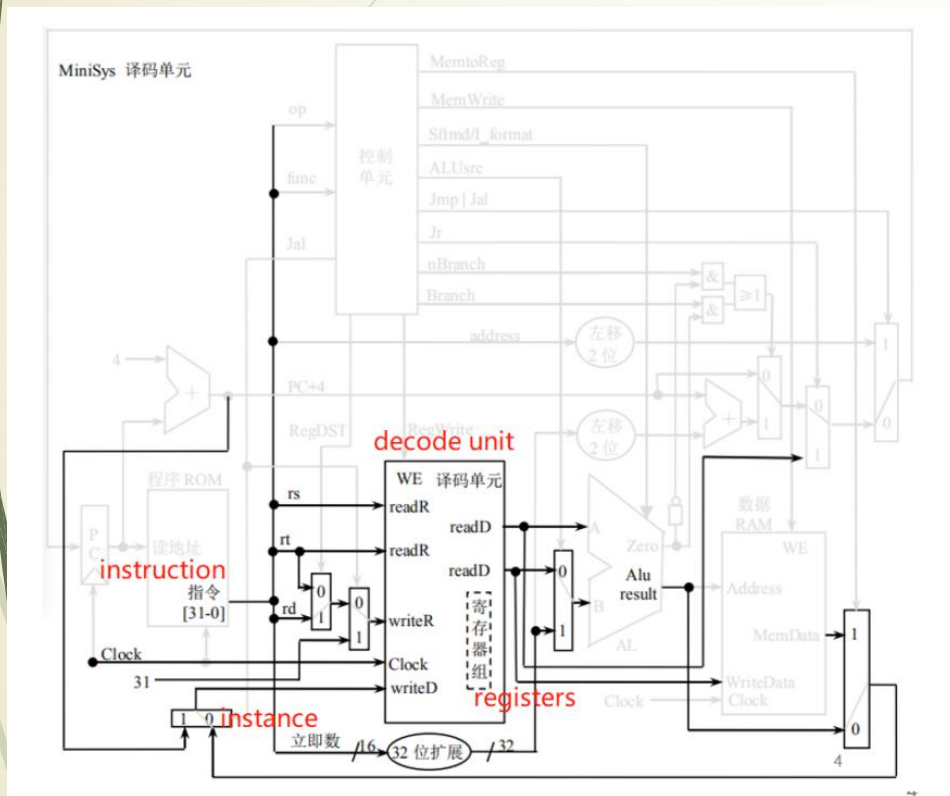

# Decoder continued
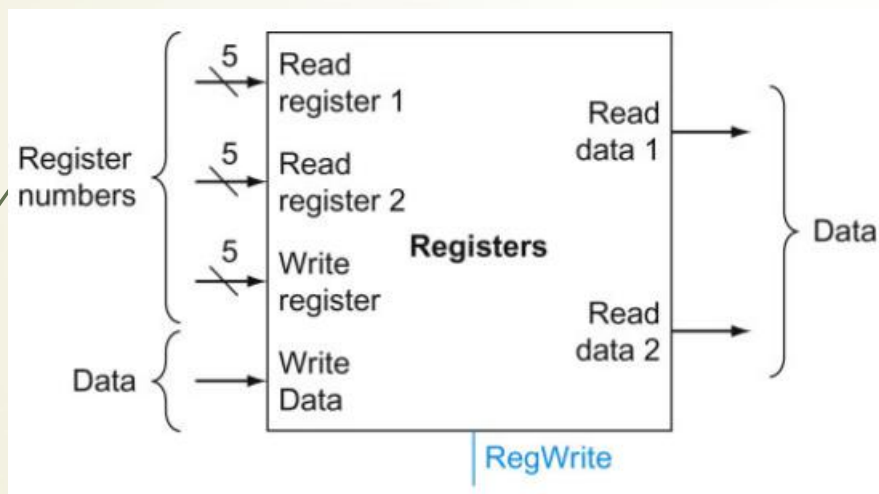
## Register File:


Almost all the instructions need to read or write register file in CPU  
32 common registers with same bitwidth: 32



```
//verilog tips:
reg[31:0] register[0:31];
assign Read data 1 = register[Read register 1]
register[Write register] <= WriteData;
```

## BASIC INSTRUCTION FORMATS

R	opcode		rs	rt		rd		shamt		funct	
	31		26 25	21 20		16 15		11 10		6 5	
I	opcode		rs		rt		immediate				
	31		26 25	21 20		16 15		0			
J	opcode		address								
	31		26 25		0						

 


Q1:

How to avoid the confliction between register read and register write?

Q2: Which kind of circuit is this register file, combinatorial circuit or sequential circuit?

 Q3: How to determine the size of address bus on register file?





# Practice1

## BASIC INSTRUCTION FORMATS


<b>R</b>	opcode	rs	rt	rd	shamt	funct
	31	26 25	21 20	16 15	11 10	6 5
<b>I</b>	opcode	rs	rt	immediate		
	31	26 25	21 20	16 15		
<b>J</b>	opcode	address				
	31	26 25				

- 1. Create the decoder as specified on page 6~7
  - There are **32** registers in the decoder, each register is **32bits** width
  - All the registers are **readable** and **writeable** except \$0, **\$0 is readonly**.
  - The **read** should be done at any time while **write** only happens on the **posedge** of the clock.
  - The register file should support **R/I/J** type instructions.
    - such as: **add, addi, lw, sw, jal, jr**
- 2. Verify its function by simulation.
- 3. List the signals which are used in the decoder

NOTE: Signals' name are determined by designer

name	from	to	bits	function
regWrite	instruction	decoder	1	1 means write the register identified by writeAdress
immediate	instruction	ALU	32	the signextended immediate
readRegister1	instruction	decoder	5	the address of read register instruction[25:21]
...				

# Memory

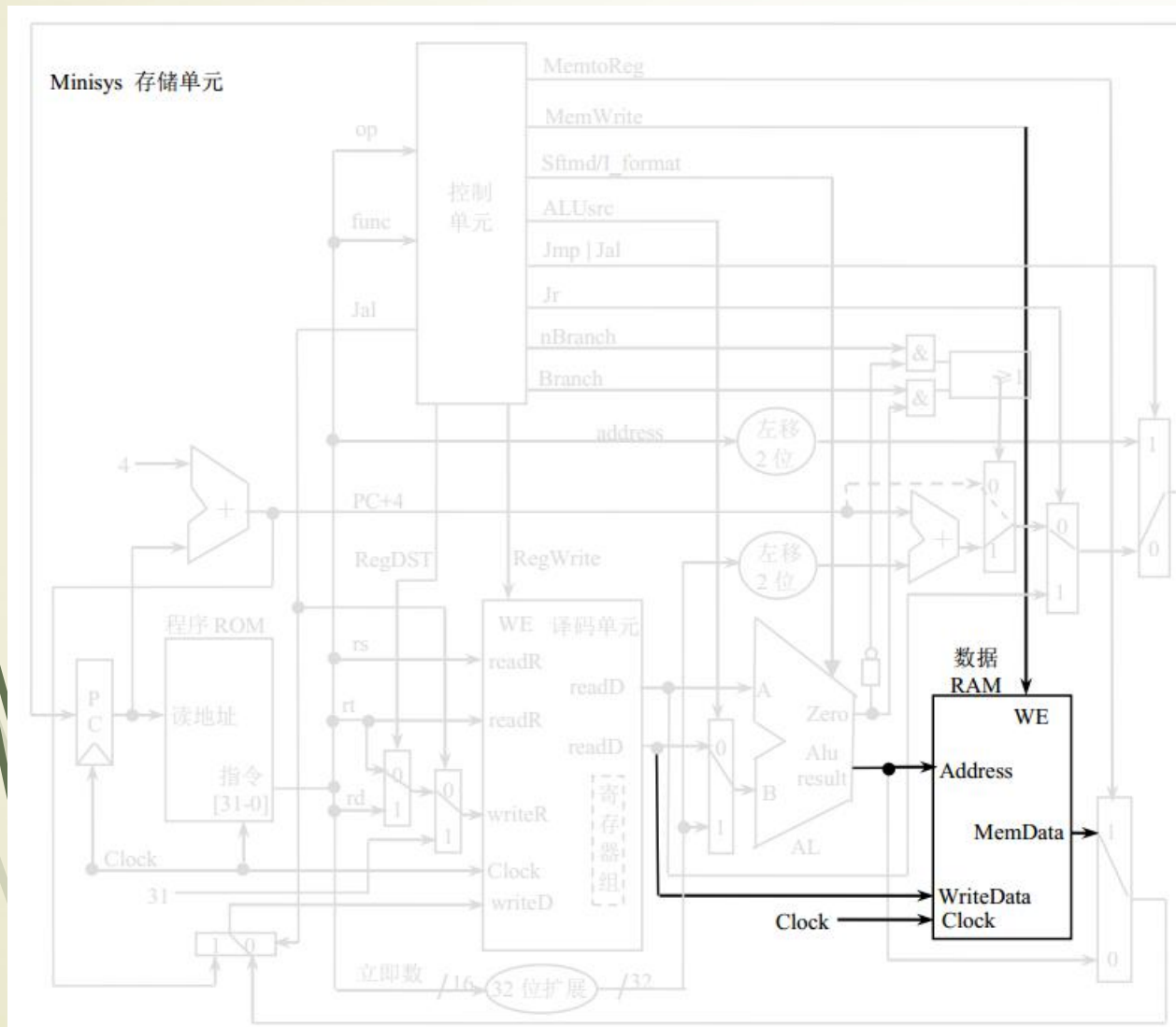

```
module dmemory32(readData,address,
writedata,memWrite,clock);
```

```
// Clock signal
input clock;
```



```
// the address of memory unit which is to be read/write
input[31:0] address;
```

```
// used to determine to write or read
input memWrite;
```

```
// data to be written into the memory unit
input[31:0] writeData;
```

```
// data to be read from memory unit
output[31:0] readData;
```

# Using IP core Block Memory

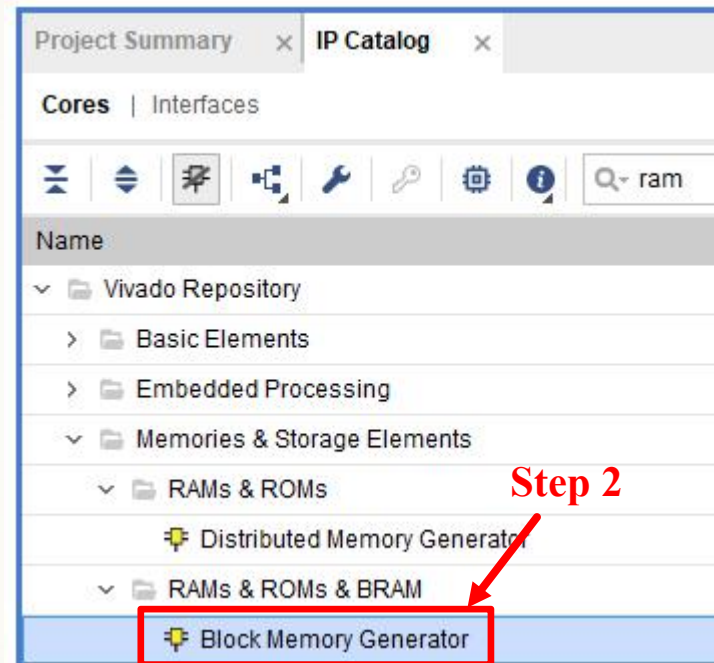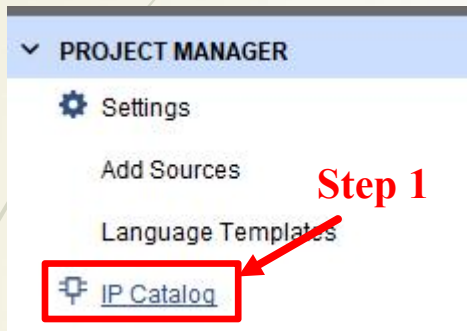

Using the IP core Block Memory from Xilinx to implement the data memory.

Import the IP core in vivado project

Step1:

in “PROJECT MANAGER” window click “IP Catalog”

Step2:

in “IP Catalog” window

- > Vivado Repository
- > Memories & Storage Elements
- > RAMs & ROMs & BRAM
- > **Block Memory Generator**

# Customize Memory IP core

Component Name: RAM

**Basic** | Port A Options | Other Options | Summary

Interface Type: Native

Memory Type: Single Port RAM

☐ Generate address interface with 32 bits

☐ Common Clock

**ECC Options**

ECC Type: No ECC

☐ Error Injection Pins: Single Bit Error Injection

**Write Enable**

☐ Byte Write Enable

Byte Size (bits): 9

**Algorithm Options**

Defines the algorithm used to concatenate the block RAM primitives. Refer datasheet for more information.

Algorithm: Minimum Area

Primitive: 8kx2

Using the IP core **Block Memory** from Xilinx to implement the data memory.

customize memory IP core:

- ▶ Component Name: **RAM**
- ▶ **Basic** settings:
  - ▶ Interface Type: **Native**
  - ▶ Memory Type: **Single-port RAM**
  - ▶ ECC options: **no ECC check**
  - ▶ Algorithm options: **Minimum area**

# Customize Memory IP core continued

Component Name

Basic | **Port A Options** | Other Options | Summary

**Memory Size**

Write Width   Range: 1 to 4608 (bits)

Read Width

Write Depth   Range: 2 to 1048576

Read Depth

Operating Mode   Enable Port Type

**Port A Optional Output Registers**

☐ Primitives Output Register ☐ Core Output Register

☐ SoftECC Input Register ☐ REGCEA Pin


**Port A Output Reset Options**

☐ RSTA Pin (set/reset pin) Output Reset Value (Hex)

☐ Reset Memory Latch Reset Priority
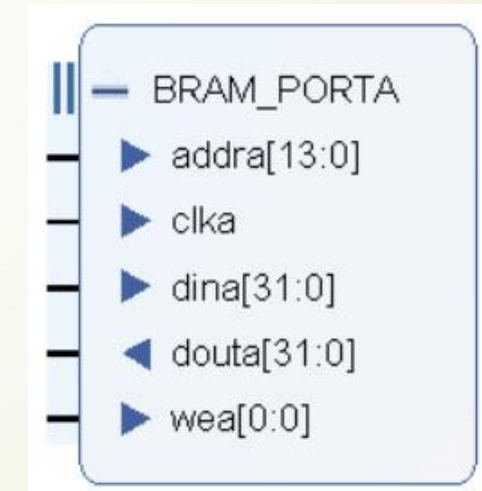
## PortA Options settings:

- Data read and write bit width: **32 bits (4Byte)**
- Write/Read Depth: **16384 (64KB)**
- Operating Mode: **Write First**
- Enable Port Type: **Always Enabled**
- PortA Optional Output Registers: **not set**



# Customize Memory IP core continued

## Other Options settings:

- 1. When specifying the initialization file for RAM, the IP core RAM just customized **WITHOUT initial file** and **corresponding path**, so set it to **no initial file** when creating RAM.
- 2. After creating the RAM
  - 2-1. **copy** the initialization file **dmem32.coe** to projectName.srscs/sources\_1/ip/RAM. ("projectName.srscs" is under the project folder)
  - 2-2. Double-click the newly created RAM IP core, **reset** it with **an initialization file**, select the **dmem32.coe** file that has been in the directory of projectName.srscs/sources\_1/ip/RAM.

Component Name: RAM

Basic | Port A Options | **Other Options** | Summary

Pipeline Stages within Mux: 0 Mux Size: 4x1

**Memory Initialization**

☐ Load Init File

Coe File: no\_coe\_file\_loaded ⓁⓇⓁ

Basic | Port A Options | **Other Options** | Summary

Pipeline Stages within Mux: 0 Mux Size: 4x1

**Memory Initialization**

☒ Load Init File

Coe File: r/project\_1/project\_1.srscs/sources\_1/ip/RAM/dmem32.coe ⓁⓇⓁ ⓁⓇⓁ

Tips: "**dmem32.coe**" file could be found in the directory "**source/lab/lab9**" of course sakai site

<https://sakai.sustech.edu.cn/portal/site/d50211ea-1586-4344-9d92-a6c42eb7f4e0/tool/b47e4c13-4220-4f61-b881-a211abee2a96?panel=Main>




# Design Module With Memory IP Instanced

```
// Part of dmemory32 module

//Generating a clk signal, which is the inverted clock of the clock signal
assign clk = !clock;

 //Create a instance of RAM(IP core), binding the ports
RAM ram (
    .clka(clk),                // input wire clka
    .wea(memWrite),           // input wire [0 : 0] wea
    .addra(address[15:2]),     // input wire [13 : 0] addra
    .dina(writeData),         // input wire [31 : 0] dina
    .douta(readData)          // output wire [31 : 0] douta
);
```



**Notes:** Because the inherent delay of the chip is used, the address line of the RAM is not ready at the rising edge of the clock, which causes the data to be read incorrectly on the rising edge of the clock. Consider the method of using the inverted clock to make the read data more ready than the address. It takes about half a clock late to get the correct address.

# Function Verification

```
//The testbench module for dmemory32
module ramTb( );
reg clock = 1'b0;
reg memWrite = 1'b0;
reg [31:0] addr = 32'h0000_0010;
reg [31:0] writeData = 32'ha000_0000;
wire [31:0] readData;

dmemory32 uram
    (clock,memWrite,addr,writeData,readData);

always
    #50 clock = ~clock;

initial begin
    #200
        writeData = 32'ha0000_00f5;
        memWrite = 1'b1;
    #200
        memWrite = 1'b0;
end
endmodule
```

The “addr” is 0x0000\_0010

1) Set “memWrite” to low level and read the data of the address in RAM.

2) Set “memWrite” to high level and writeData to 0xa000\_00f5

3) Set “memWrite” to low level and read the data of the address in RAM.




# Function Verification continued

```

1 memory_initialization_radix = 16;
2 memory_initialization_vector =
3 007f2812,
4 007f2811,
5 007f2810,
6 007f2810,
7 007f280f,
8 00000001,
9 00000002,
10 00000003,
11 00000005,
12 00000006,
13 00000007,
14 0000ffff,
15 00000000,
16 00000000,

```

Name	Value
> addr[31:0]	00000010
> writeData[31:0]	000000f5
memWrite	0
clock	0
> readData[31:0]	000000f5

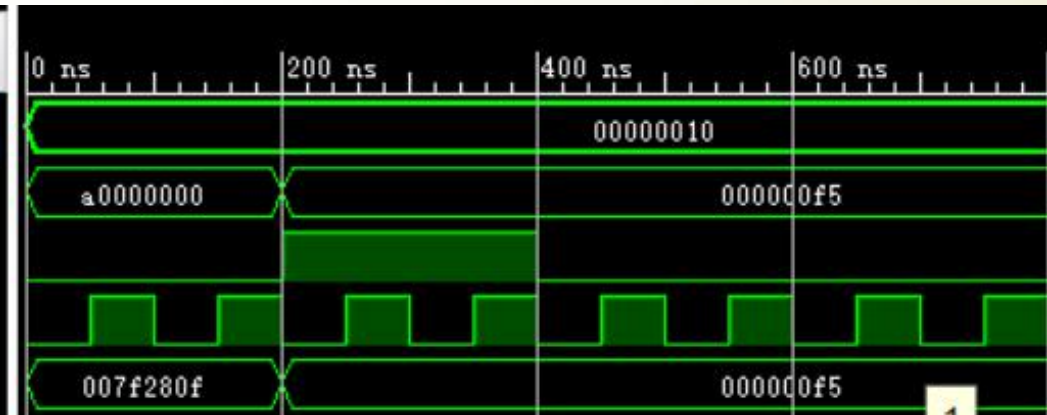

Q1: On which edge of clock does the read and write operations occur? posedge or negedge?

Q2: What's value will be get while read the memory according to the "addr" 0x0000\_0016?

Tips: "dmem32.coe" file could be found in the directory "source/lab/lab9" of course sakai site

<https://sakai.sustech.edu.cn/portal/site/d50211ea-1586-4344-9d92-a6c42eb7f4e0/tool/b47e4c13-4220-4f61-b881-a211abee2a96?panel=Main>

## Practice2

- 1. Build the data memory module following the steps list on page 11~15  
NOTE: Using the same “dmem32.coe” as page 17 to initialize the memory ip core.
- 2. Verify its function by simulation
  - Change the testbench by adding more testing
    - **Read** the values one by one from memory unit where are specified in the red box of the screenshot on the right hand.
    - Write a word(value is 0x1000\_0000) to the memory unit where is specified in the blue box of the screenshot on the left hand, then read it out.
- 3. List all the signals which are needed for data memory module

```

1 memory_initialization_radix = 16;
2 memory_initialization_vector =
3 007f2812,
4 007f2811,
5 007f2810,
6 007f2810,
7 007f280f,
8 00000001,
9 00000002,
10 00000003,
11 00000005,
12 00000006,
13 00000007,
14 0000ffff,
15 00000000,
16 00000000,
17 00000000,
18 00000000,
19 00000000,
20 00000000,
21 00000000,

```

read these initial value


write this word with 0x1000\_0000 then read it

name	from	to	bits	function
clock		Data Memory	1	memory write is sensitive with its negedge
rdata	Data Memory	Decoder	32	the word read from the data memory and send to decoder
...				

Tips: “dmem32.coe” file could be found in the directory “source/lab/lab9” of course sakai site

<https://sakai.sustech.edu.cn/portal/site/d50211ea-1586-4344-9d92-a6c42eb7f4e0/tool/b47e4c13-4220-4f61-b881-a211abee2a96?panel=Main>

# TIPS: Control path & Data path of CPU

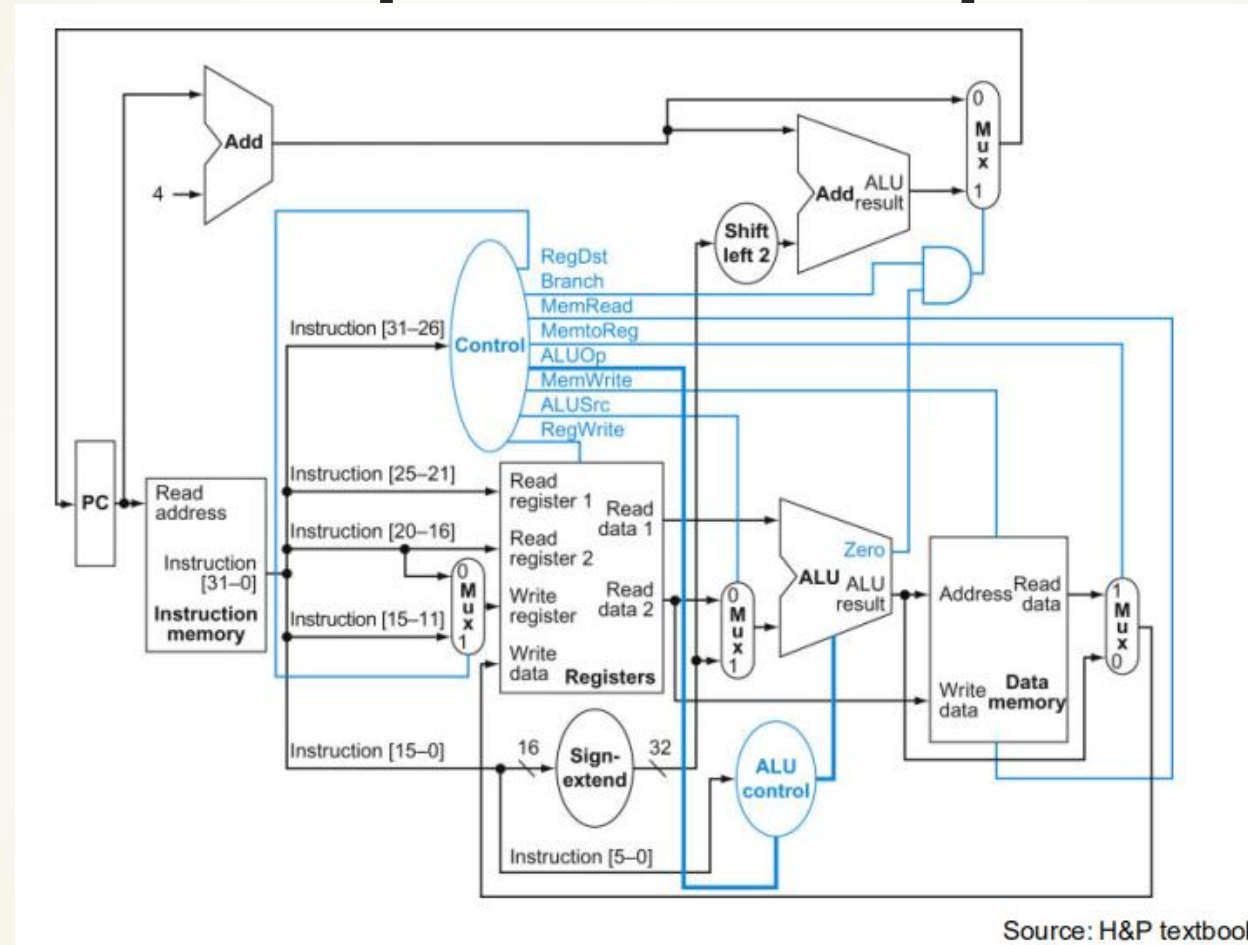

**Control Path:** Interpret instructions and generate signals to control the data path to execute instructions

**Data Path:** The parts in CPU with components which are involved to execute instructions